



MP Controller For High Performance Process Power Supplies

FEATURES

- Runs on 3.3- or 5-V Supplies
- Adjustable, High Precision Output Voltage
- High Frequency Operation (>1 MHz)
 Full Set of Protection Circuitry
- High Efficiency Synchronous Switching
- 2000-V ESD Rating (Si9140CQ/DQ)

DESCRIPTION


Siliconix' Si9140 Buck converter IC is a high-performance. surface-mount switchmode controller made to power the new generation of low-voltage, high-performance microprocessors. The Si9140 has an input voltage range of 3 to 6.5 V to simplify power supply designs in desktop PCs. Its high-frequency switching capability and wide bandwidth feedback loop provide tight, absolute static and transient load regulation. Circuits using the Si9140 can be implemented with low-profile, inexpensive inductors, and will dramatically minimize power supply output and processor decoupling capacitance. The Si9140 is designed to meet the stringent regulation requirements of new and future high-frequency microprocessors, while improving the overall efficiency in new "green" systems.

Today's state-of-the-art microprocessors run at frequencies over 100 MHz. Processor clock speeds are going up and so are current requirements, but operating voltages are going down. These simultaneous changes have made dedicated, high-frequency, point-of-use buck converters an essential part of any system design. These point-of-use converters must operate at higher frequencies and provide wider feedback bandwidths than existing converters, which typically operate at less than 250 kHz and have feedback bandwidths of less than 50 kHz. The Si9140's 100-kHz feedback loop bandwidth ensures a minimum improvement of one-half the required output/decoupling capacitance, resulting in a tremendous reduction in board size and cost of implementation.

With the microprocessing power of any PC representing an investment of hundreds of dollars, designers need to ensure that the reliable operation of the processor will not be affected by the power supply. The Si9140 provides this assurance. A demo board, the Si9140DB, is available.

Si9140CQ-T1 and Si9140DQ-T1 are available in lead free.

APPLICATION CIRCUIT

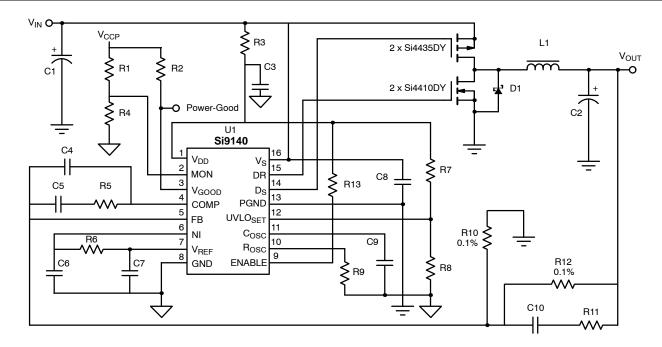



ABSOLUTE MAXIMUM RATINGS

Voltages Referenced to GND.		
V _{DD} , V _S Pgnd		Thermal Impedance ($\Theta_{ m JA}$) 16-Pin SOIC (Y Suffix)
V _{DD} to V _S		16-Pin TSSOP (Q Suffix)
Logic Inputs	350 mA	Operating Temperature 0° to 70°C D Suffix -40° to 85°C
Operating Junction Temperature	900 mW	Notes a. Device mounted with all leads soldered or welded to PC board. b. Derate 7.2 mW/°C above 25°C. c. Derate 7.4 mW/°C above 25°C.

RECOMMENDED OPERATING RANGE

es Reterenced to GND.		
3 V to 6.5 V	C _{OSC}	47 pF to 200 pF
3 V to 6.5 V	Linear Inputs	0 to V _{DD}
	Digital Inputs	0 to V _{DD}
	V _{REF} Load Resistance	>150 kΩ
	% Heferenced to GND. $ 3 \ V \ to \ 6.5 \ V \\ 3 \ V \ to \ 6.5 \ V \\ 20 \ \text{kHz} \ to \ 2 \ \text{MHz} \\ 5 \ \text{k}\Omega \ to \ 250 \ \text{k}\Omega $	

SPECIFICATIONS						
		Test Conditions Unless Otherwise Specified ^a 3 V ≤ V _{DD} ≤ 6.5 V, V _{DD} = V _S	Limits C Suffix 0 to 70°C D Suffix -40 to 85°C			
Parameter	Symbol	$GND = P_{GND}$	Min ^b	Тур	Max ^b	Unit
Reference						•
0.44)/-4	.,	I _{REF} = -10 μA	1.455		1.545	V
Output Voltage	V _{REF}	T _A = 25°C	1.477	1.50	1.523	7 °
Oscillator						
Maximum Frequency ^c	f _{MAX}	V_{DD} = 5 V, C_{OSC} = 47 pF, R_{OSC} = 5.0 k Ω	2.0			
Accuracy	fosc	V_{DD} = 5 V C_{OSC} = 100 pF, R_{OSC} = 7.50 k Ω , T_A = 25°C	0.85	1.0	1.15	MHz
R _{OSC} Voltage	V _{ROSC}			1.0		V
Voltage Stability ^c	Δf/f	$4 \text{ V} \leq \text{V}_{DD} \leq 6 \text{ V}$, Ref to 5 V , $\text{T}_{A} = 25^{\circ}\text{C}$	-8		8	- %
Temperature Stability ^c	Δ1/1	Referenced to 25°C		±5		
Error Amplifier (C _{OSC} =	GND, OSC DISA	BLED)				
Input Bias Current	I _{FB}	$V_{NI} = V_{REF}$, $V_{FB} = 1.0 V$	-1.0		1.0	μΑ
Open Loop Voltage Gain	A _{VOL}		47	55		dB
Offset Voltage	V _{OS}	V _{NI} = V _{REF}	-15	0	15	mV
Unity Gain Bandwidthc	BW			10		MHz
0.4.4.0		Source (V _{FB} = 1 V, NI = V _{REF})		-2.0	-1.0	4
Output Current	l _{EA}	Sink (V _{FB} = 2 V, NI = V _{REF})	0.4	0.8		mA
Power Supply Rejection ^c	P _{SRR}	3 V < V _{DD} < 6.5 V		60		dB
UVLO _{SET} Voltage Monit	or					
	V _{UVLOHL}	UVLO _{SET} High to Low	0.85	1.0		
Under Voltage Lockout	V _{UVLOLH}	UVLO _{SET} Low to High		1.2		v
Hysteresis	V _{HYS}	V _{UVLOLH –} V _{UVLOHL}		175		mV


^{* .} Exposure to Absolute Maximum rating conditions for extended periods may affect device reliability. Stresses above Absolute Maximum rating may cause permanent damage. Functional operation at conditions other than the operating conditions specified is not implied. Only one Absolute Maximum rating should be applied at any one time




SPECIFICATIONS						
		Test Conditions Unless Otherwise Specified ^a	Limits C Suffix 0 to 70°C D Suffix -40 to 85°C			
Parameter	Symbol	$3 \text{ V} \leq \text{V}_{DD} \leq 6.5 \text{ V}, \text{V}_{DD} = \text{V}_{S}$ $\text{GND} = \text{P}_{\text{GND}}$	Minb	Тур	Max ^b	Unit
UVLO _{SET} Voltage Monitor	<u> </u>		•			1
UVLO Input Current	I _{UVLO(SET)}	$V_{UVLO} = 0$ to V_{DD}	-100		100	nA
Output Drive (D _R and D _S)						
Output High Voltage	V _{OH}	$V_S = V_{DD} = 5 \text{ V}, I_{OUT} = -10 \text{ mA}$	4.7	4.8		.,
Output Low Voltage	V _{OL}	$V_S = V_{DD} = 5 \text{ V}, I_{OUT} = 10 \text{ mA}$		0.2	0.3	V
Peak Output Current	I _{SOURCE}	$V_{S} = V_{DD} = 5 \text{ V}, V_{OUT} = 0 \text{ V}$		-380	-260	
Peak Output Current	I _{SINK}	$V_{S} = V_{DD} = 5 \text{ V}, V_{OUT} = 5 \text{ V}$	200	300		mA
Break-Before-Make	t _{BBM}	V _{DD} = 6.5 V		40		nS
Logic	<u> </u>		•		•	
ENABLE Turn-On Delay	t _{dEN}	ENABLE Delay to Output, EN _{LH} , V _{DD} = 5 V		1.5		μs
ENABLE Logic Low	V _{ENL}				0.2 V _{DD}	.,
ENABLE Logic High	V _{ENH}		0.8 V _{DD}			- V
ENABLE Input Current	I _{EN}	ENABLE = 0 to V _{DD}	-1.0		1.0	μΑ
V _{GOOD} Comparator (Voltage	ge-Good Com	parator)				
Input Offset Voltage	Vos		-45	0	45	.,
Input Hysteresis	V _{INHYS}	V_{IN} Common Mode Voltage = V_{REF} , V_{DD} = 5 V		10		mV
Input Bias Current	I _{BMON}	$V_{IN} = V_{REF}, V_{DD} = 5 V$	-1	0	1	μΑ
Output Sink I	I _{SINK}	V _{OUT} = 5 V, V _{DD} = 5 V	6	9		mA
Output Low Voltage	V _{OL}	$I_{OUT} = 2 \text{ mA}, V_{DD} = 5 \text{ V}$		350	500	mV
Supply	•		•			
Supply Current—Normal Mode	Ι. Ι	f_{OSC} = 1 MHz, R_{OSC} = 7.50 k Ω		1.6	2.3	mA
Supply Current—Standby Mode	l _{DD}	ENABLE < 0.4 V		250	330	μΑ

Notes
a. 100 pF includes C_{STRAY} on C_{OSC}.
b. The algebraic convention whereby the most negative value is a minimum and the most positive a maximum, is used in this data sheet.

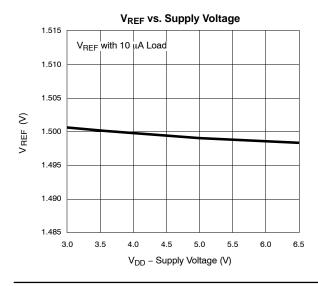
TYPICAL CHARACTERISTICS (25°C UNLESS OTHERWISE NOTED)




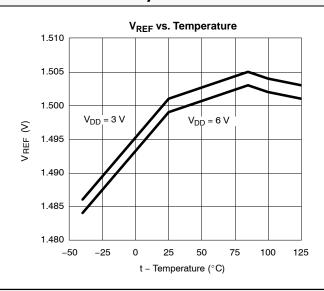





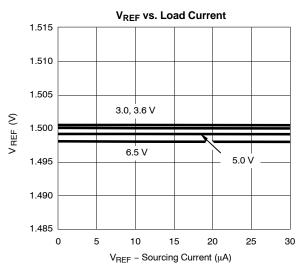
TYPICAL CHARACTERISTICS (25°C UNLESS OTHERWISE NOTED)




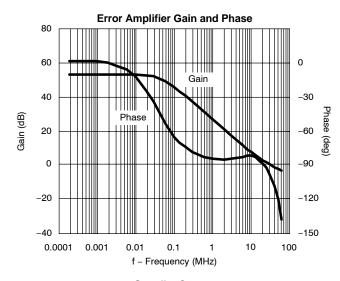

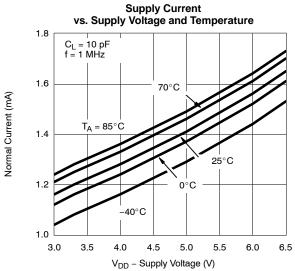

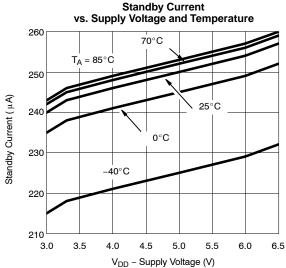


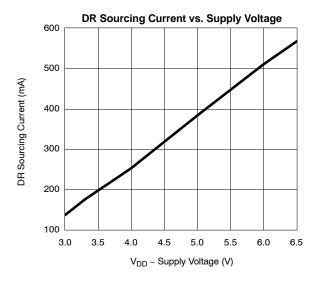


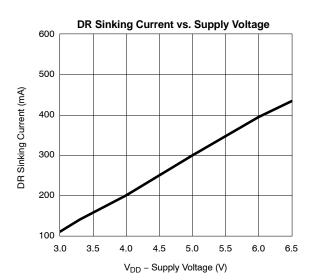





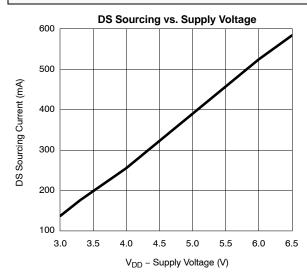
TYPICAL CHARACTERISTICS (25°C UNLESS OTHERWISE NOTED)




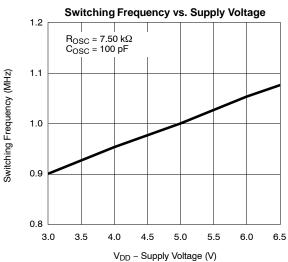

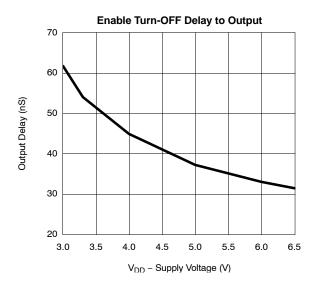

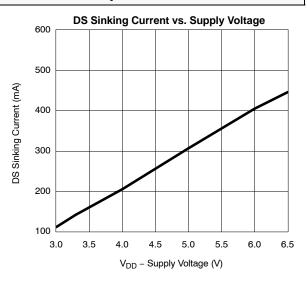


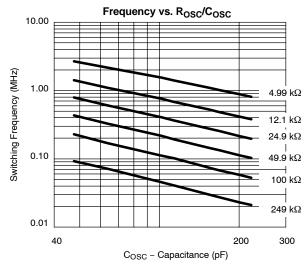

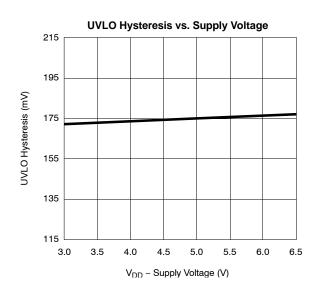





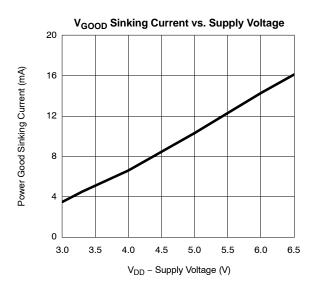TYPICAL CHARACTERISTICS (25°C UNLESS OTHERWISE NOTED)



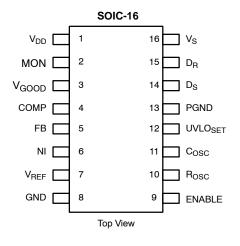PIN CONFIGURATIONS AND ORDERING INFORMATION



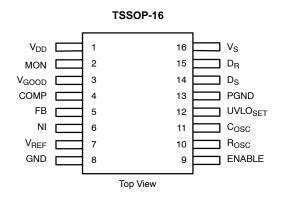

ORDERING INFORMATION-SOIC-16			
Part Number Temperature Range			
Si9140CY			
Si9140CY-T1	0° to 70°C		
Si9140CY-T1—E3			
Si9140DY			
Si9140DY-T1	−40° to 85°C		
Si9140DY-T1—E3			

ORDERING INFORMATION—TSSOP-16				
Part Number Temperature Range				
Si9140CQ				
Si9140CQ-T1	0° to 70°C			
Si9140CQ-T1—E3				
Si9140DQ				
Si9140DQ-T1	−40° to 85°C			
Si9140DQ-T1—E3				



PIN DESCRIPTION

Pin 1: V_{DD}

The positive power supply for all functional blocks except output driver. A bypass capacitor of 0.1 μF (minimum) is recommended.

Pin 2: MON

Non-inverting input of a comparator. Inverting input is tied internally to reference voltage. This comparator is typically used to monitor the output voltage and to flag the processor when the output voltage falls out of regulation.

Pin 3: V_{GOOD}

This is an open drain output. It will be held at ground when the voltage at MON (Pin 2) is less than the internal reference. An external pull-up resistor will pull this pin high if the MON pin (Pin 2) is higher than the $V_{\rm RFF}$. (Refer to Pin 2 description.)

Pin 4: COMP

This pin is the output of the error amplifier. A compensation network is connected from this pin to the FB pin to stabilize the system. This pin drives one input of the internal pulse width modulation comparator.

Pin 5: FB

The inverting input of the error amplifier. An external resistor divider is connected to this pin to set the regulated output voltage. The compensation network is also connected to this pin.

Pin 6: NI

The non-inverting input of the error amplifier. In normal operation it is externally connected to $V_{\mbox{\scriptsize REF}}$ or an external reference.

Pin 7: V_{REF}

This pin supplies a 1.5-V reference.

Pin 8: GND (Ground)

Pin 9: ENABLE

A logic high on this pin allows normal operation. A logic low places the chip in the standby mode. In standby mode normal operation is disabled, supply current is reduced, the oscillator stops and D_S goes high while D_R goes low.

Pin 10: Rosc

A resistor connected from this pin to ground sets the oscillator's capacitor C_{OSC} , charge and discharge current. See the oscillator section of the description of operation.

Pin 11: Cosc

An external capacitor is connected to this pin to set the oscillator frequency.

$$f_{OSC} \simeq \frac{0.75}{R_{OSC} \times C_{OSC}} \qquad \text{ (at V}_{DD} = 5.0 \text{ V)}$$

Pin 12: UVLO_{SET}

This pin will place the chip in the standby mode if the $UVLO_{SET}$ voltage drops below 1.2 V. Once the $UVLO_{SET}$ voltage exceeds 1.2 V, the chip operates normally. There is a built-in hysteresis of 165 mV.

Pin 13: PGND

The negative return for the V_S supply.

Pin 14: Ds

This CMOS push-pull output pin drives the external p-channel MOSFET. This pin will be high in the standby mode. A break-before-make function between $D_{\rm S}$ and $D_{\rm R}$ is built-in.

Pin 15: D_R


This CMOS push-pull output pin drives the external n-channel MOSFET. This pin will be low in the standby mode. A break-before-make function between the $D_{\rm S}$ and $D_{\rm R}$ is built-in.

Pin 16: V_S


The positive terminal of the power supply which powers the CMOS output drivers. A bypass capacitor is required.



FUNCTIONAL BLOCK DIAGRAM

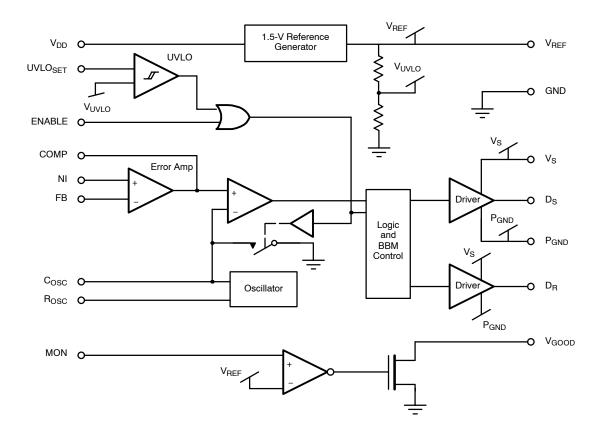

TIMING WAVEFORMS

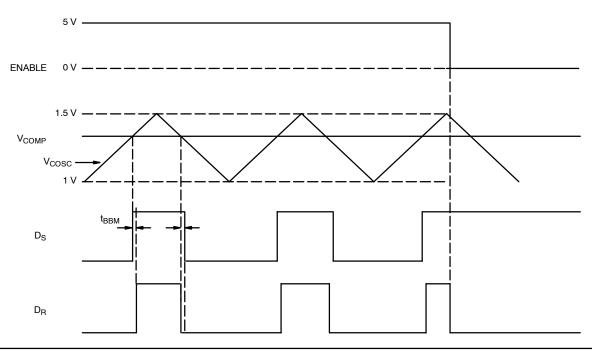





DESCRIPTION OF OPERATION


Schematics of the Si9140 dc-to-dc conversion solutions for high-performance PC microprocessors are shown in Figure 1 and 2 respectively. These solutions are geared to meet the extremely demanding transient regulation and power requirements of these new microprocessors at minimal cost

and with a minimal parts count. The two solutions are nearly identical, except for slight variations in output voltage, load transient amplitude, and specified power. Figure 3 is a schematic diagram for a 3.3-V logic converter.

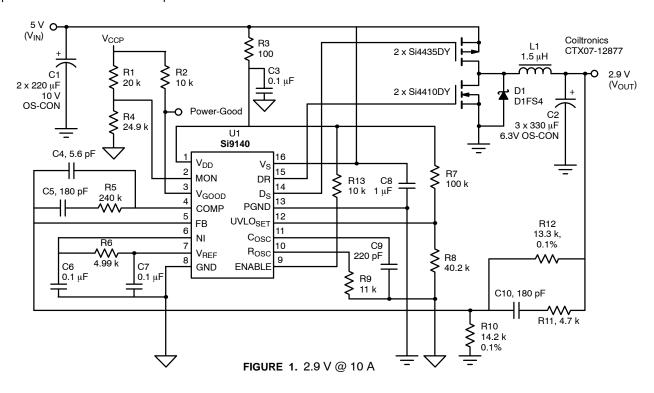

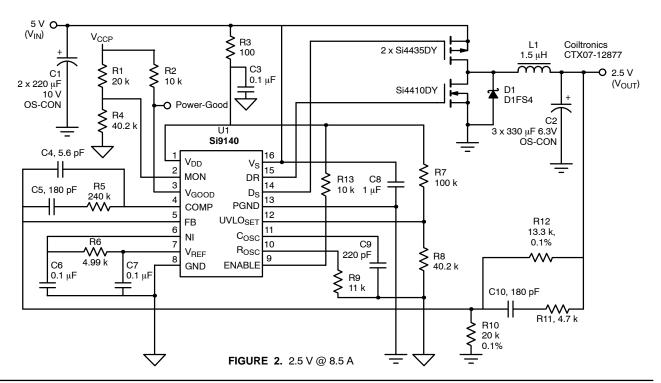



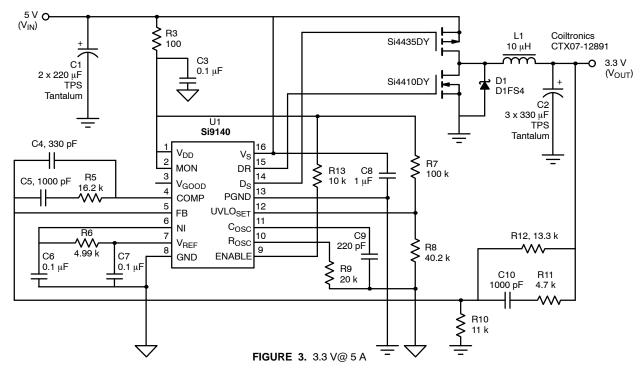

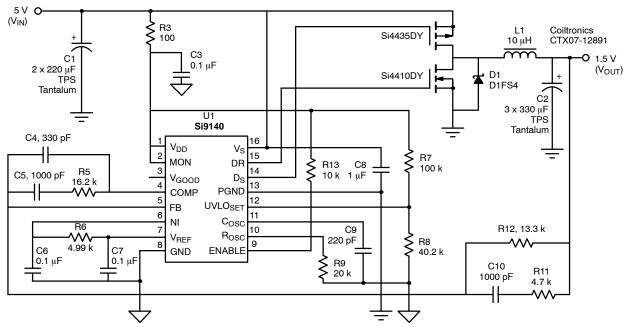


FIGURE 4. 1.5-V Converter for GTL+ Bus @ 5 A

Figure 4 is a schematic diagram of a converter which produces 1.5 V for a GTL bus.

Each of these dc-to-dc converters has four major sections:

PWM Controller—regulates the output voltage

- Switch and Synchronous Rectification MOSFETs—delivers the power to the load
- Inductor—filters and stores the energy
- Input/Output Capacitor—filters the ripple



The functions of each circuit are explained in detail below. Design equations are provided to optimize each application circuit.

PWM Controller

There are generally two types of controllers, voltage mode or current mode. In voltage mode control, an error voltage is generated by comparing the output voltage to the reference voltage. The error voltage is then compared to an artificial ramp, and the result is the duty cycle necessary to regulate the output voltage. In current mode, an actual inductor current is used, in place of the artificial ramp, to sense the voltage across the current sense resistor.

The logic and timing sequence for voltage mode control is shown in Figure 5. The Si9140 offers voltage mode control, which is better suited for applications requiring both fast transient response and high output current.

Current mode control requires a current sense resistor to monitor the inductor current. A 10-m Ω sense resistor in a 10-A design will dissipate 1 W, decreasing efficiency by 3.5%. Such a design would require a 2-W resistor to satisfy derating criteria, besides requiring additional board space. Voltage mode control is a second-order LC system and has a faster natural transient response compared to current mode control (first-order RC system). Current mode has the advantage of providing an inherently good line regulation. But the situations where line voltage is fixed, as in the point-of-use conversion for microprocessors, this feature is wasted. Current mode control also provides automatic pulse-to-pulse current limiting. This feature requires a current sense resistor as stated above. These characteristics make voltage mode control ideal for high-end microprocessor power supplies.

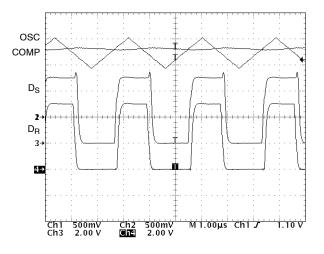


FIGURE 5. Voltage Mode Logic and Timing Diagram

The error amplifier of the PWM controller plays a major role in determining the output voltage, stability, and the transient response of the power supply. In the Si9140, the non-inverting input of the error amplifier is available for use with an external precision reference for tighter tolerance regulation. With a two-pair lead-lag compensation network, it is easy to create a stable 100-kHz closed loop converter with the Si9140 error amplifier.

The Si9140 achieves the $5-\mu S$ transient response by generating a 100-kHz closed-loop bandwidth. This is possible only by switching above 400 kHz and utilizing an error amplifier with at least a 10-MHz bandwidth. The Si9140 controller has a 25-MHz unity gain bandwidth error amplifier. The switching frequency must be at least four times greater than the desired closed-loop bandwidth to prevent oscillation. To respond to the stimuli, the error amplifier bandwidth needs to be at least 10 times larger than the desired bandwidth.

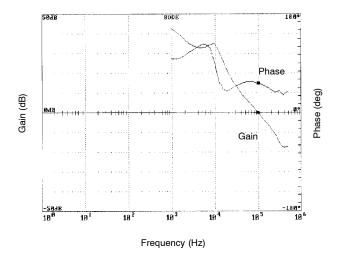


FIGURE 6. 100-kHz BW Synchronous Buck Converter

The Si9140 solution requires only three 330- μ F OS-CON capacitors on the output of power supply to meet the 10-A transient requirement. Other converter solutions on the market with 20- to 50-kHz closed loop bandwidths typically require two to five times the output capacitance specified above to match the Si9140's performance.

The theoretical issues and analytical steps involved in compensating a feedback network are beyond the scope of this application note. However, to ease the converter design for today's high-performance microprocessors, typical component values for the feedback network are provided in Table 1 for various combinations of output capacitance. Figure 6 shows the Bode plot (frequency domain) of the 2.9-V converter shown schematically in Figure 1.

TABLE 1. FEEDBACK NETWORK COMPONENT VALUES					
Total Output and Decoupling Capacitance C4 C5 R5					
$\begin{array}{cccccccccccccccccccccccccccccccccccc$	5.6 pF	180 pF	240 k		
$\begin{array}{cccccccccccccccccccccccccccccccccccc$	10 pF	220 pF	200 k		
$\begin{array}{cccccccccccccccccccccccccccccccccccc$	10 pF	100 pF	100 k		


a. Power supply output capacitance.

Figure 7 is the measured transient response (time domain) for the 10-A step response. The measured transient response shows the processor voltage regulating to 70 mV, well within the 0.145-V regulation.

The Si9140's switching frequency is determined by the external R_{OSC} and C_{OSC} values, allowing designers to set the switching frequency of their choice. For applications where space is the main constraint, the switching frequency can be set as high as 2 MHz to minimize inductor and output capacitor size. In applications where efficiency is the main concern, the switching frequency can be set low to maximize battery life. The switching frequency for high-performance processors applications circuits are set for 400 kHz. The equation for switching frequency is:

$$f_{OSC} \approx \frac{0.75}{R_{OSC} \times C_{OSC}}$$
 (at $V_{DD} = 5.0 \text{ V}$)

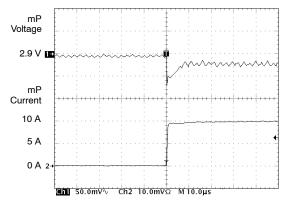The precision reference is set at $1.5\,V\pm1.5\%$. The reference is capable of sourcing up to 1 mA. The combination of 1.5%



a) Transient Response from 0- to 10-A Step Load




reference and 3.5% transient load regulation safely complies with the $\pm 5\%$ regulation requirement. If additional margin is desired, an external precision reference can be used in place of the internal 1.5-V reference.

Switching and Synchronous Rectification MOSFETs

The synchronous gate drive outputs of Si9140 PWM controller drive the high-side p-channel switch MOSFET and the low-side n-channel synchronous rectifier MOSFET. The physical difference between the non-synchronous to synchronous rectification requires an additional MOSFET across the free-wheeling diode (D1). The inductor current will reach 0 A if the peak-to-peak inductor current equals twice the output current. In synchronous rectification mode, current is allowed to flow backwards from the inductor (L1) through the synchronous MOSFET (Q3) and to the output capacitor (C2) once the current reaches 0 A. Refer to schematic on Figure 1. In non-synchronous rectification, the diode (D1) prevents the current from flowing in the reverse direction. This minor difference has a drastic affect on the performance of a power supply. By allowing the current to flow in the reverse direction, it preserves the continuous inductor current mode, maintaining the wide converter bandwidth and improving efficiency. Also, maintaining the continuous current mode during light load to full load guarantees consistent transient response throughout a wide range of load conditions.

The transition from stop clock and auto halt to active mode is a perfect example. The microprocessor current can vary from 0.5 A to 10 A or greater during these transitions. If the converter were to operate in discontinuous current mode during the stop clock and auto halt modes, the transfer function of the converter would be different compared to operation in the active mode. In discontinuous current mode, the converter bandwidth can be 10 to 15 times lower than the continuous current mode (Figure 8). Therefore, the response time will also be 10 to 15 times slower, violating the microprocessor's regulator requirements. This could result in unreliable operation of the microprocessor.

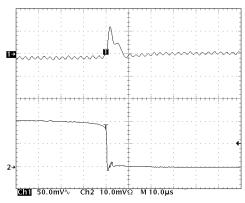

b) Transient Response from 10- to 0-A Step Load

FIGURE 7.

b. μprocessor decoupling capacitance.



For these reasons, synchronous rectification is a must in today's microprocessors power supply design. Pulse-skipping modes are undesirable in high-performance microprocessor power supplies, especially when the minimum load current is as high as 500 mA. This pulse-skipping mode disables the synchronous rectification during light load and generates a random noise spectrum which may produce EMI problems.

Siliconix' TrenchFET technology has resulted in 20-m Ω n-channel (Si4410DY) and 35-m Ω p-channel (Si4435DY) MOSFETs in the SO-8 surface-mount package. These LITTLE FOOT® products totally eliminate the need for an external heatsink.

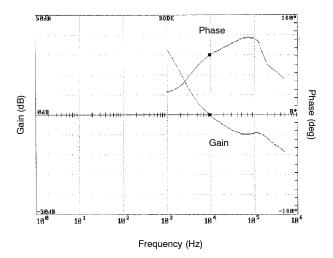


FIGURE 8. Non-Synchronous Converter BW

Worst case current of 10 A can be handled with two paralleled Si4435DY and two paralleled Si4410DY MOSFETs, which results in the efficiency levels shown in Figure 9.

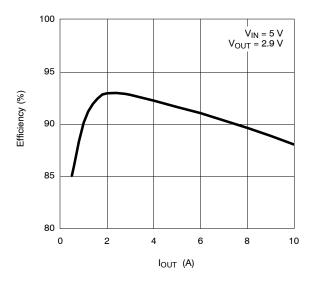


FIGURE 9. Efficiency

Good electrical designs must provide an adequate margin for the specification, but they should not be grossly overdesigned to lower costs. LITTLE FOOT power MOSFETs allow designers to balance cost and performance considerations without sacrificing either. If the design requires only an 8.5-A continuous current, for example, one Si4410DY can be eliminated. Table 2 shows the number of MOSFETs required to handle the various output current levels of today's high-performance microprocessors. For other output power levels, the equations below should be used to calculate the power handling capability of the MOSFET.

	TABLE 2. CONVERTER REQUIREMENTS (FIGURES 1, 2, AND 3)					
I _O (A) Maxi- mum Quantity High-Side P-Channel Si4435DY Quantity Low-Side N-Channel Si4410DY Quantity Input (C1 Capacitor Os-con 2						
5 A	1	1	1			
8.5 A	2	1	2			
10 A	2	2	2			
14.5 A	3	2	3			



$${\rm P_{Dissipation} \ in \ switch} = {\rm I_{RMS \ SW}}^2 \times {\rm R_{SW}} + \frac{{\rm Q_{SW} \times V_{IN} \times f_{OSC}}}{2} + \frac{{\rm I_{PP} \times V_O \times \tau_C \times f_{OSC}}}{2}$$

$$I_{\text{RMS SW}} = \sqrt{\left(I_{\text{PEAK}}^2 + I_{\text{PP}}^2 + I_{\text{PEAK}} \times I_{\text{PP}}\right) \times \frac{V_{\text{O}}}{3 \times V_{\text{IN}}}}$$

$${\rm P_{Dissipation}} \text{ in synchronous rectification } = {\rm I_{RMS}} \underset{RECT}{{\rm RECT}}^2 \times {\rm R_{RECT}} + \frac{{\rm Q_{RECT}} \times {\rm V_{IN}} \times {\rm f_{OSC}}}{2}$$

$$I_{RMS\;RECT} = \sqrt{\left(I_{PEAK}^{2} + I_{PP}^{2} + I_{PEAK} \times I_{PP}\right) \times \frac{(V_{IN} - V_{O})}{3 \times V_{IN}}}$$

$$I_{PP} = I_{PFAK} + \Delta I$$

$$\Delta I = \frac{{V_O}^2}{L \times f_{OSC} \times V_{IN}}$$

$$I_{PEAK} = \frac{P_{IN} - (0.5 \times V_O \times \Delta I)}{V_O}$$

$$P_{IN} = \frac{V_O \times I_O}{n}$$

I_{RMSSW} = Switch rms current R_{SW} = Switch on resistance


 $I_{RMSRECT}$ = Synchronous rectifier rms current R_{RECT} = Synchronous rectifier on resistance

Q_{SW} = Total gate charge of switch

Q_{RECT} = Total gate charge of synchronous rectifier

 V_{IN} = Input voltage V_{O} = Output voltage I_{O} = Output current I_{OSC} = Switching frequency

 η = efficiency τ_C = Crossover time

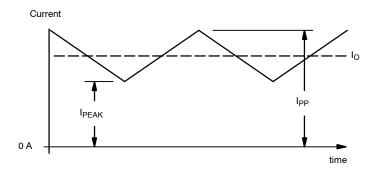

Inductor

The size and value of the inductor are critical in meeting overall circuit dimensional requirements and in assuring proper transient voltage regulation. The size of the core is determined by the output power, the material of the core, and the operating frequency. To handle higher output power, the core must be larger. Luckily, a higher switching frequency will lower the inductance value, decreasing the core size. However, a higher switching frequency can also mean greater core loss.

In applications where the dc flux density is high and the ac flux density swing is only 100 to 200 gauss, the core loss will be

negligible compared to the wire loss. Kool Mu is the best material to use at 500 kHz to deliver 30 W in the minimum volume. Ferrite has a lower core cost and loss at this frequency, but the core size is fairly large. If the power supply is designed on the motherboard and space is not a critical issue, ferrite is a better choice.

The higher switching frequency reduces the core size by decreasing the amount of energy that must be stored between switching periods. It also accelerates the transient response to the load by decreasing the inductance value. The inductance is calculated with following equation:





$$L = \frac{V_0^2}{V_{IN} \times \Delta I \times f_{OSC}}$$

 ΔI = desired output current ripple. Typically ΔI = 25% of maximum output current.

Finally, the time required to ramp up the current in the inductor can be reduced with smaller inductance. A quick response from the power supply relaxes the decoupling capacitance required at the microprocessor, reducing the overall solution cost and size.

Input Capacitor

The input capacitor's function is to filter the raw power and serve as the local power source to eliminate power-up and transient surge failures. The type and characteristics of input capacitors are determined by the input power and inductance of the step-down converter. The ripple current handling requirement usually dominates the selection criteria. The capacitance required to maintain regulation will automatically be achieved once it meets the ripple current requirement. The following equation calculates the ripple current of the input capacitor:

$$I_{\text{RIPPI E}} = \sqrt{I_{\text{RMSSW}}^2 - I_{\text{IN}}^2}$$

An aluminum-electrolytic capacitor from Sanyo (OS-CON), AVX (TPS Tantalum), or Nichicon (PL series) should be used in high-power (30-W) applications to handle the ripple current. The Sanyo capacitor is smaller and handles higher ripple current than Nichicon, but at higher cost than the Nichicon product. The AVX Tantalum capacitor has the best capacitance and current handling capability per volume ratio, but it takes extra surface area compared to OS-CON or PL series. The TPS capacitors, lead time and cost have increased drastically in the recent past due to high demand, causing designers to shy away from the TPS Tantalum capacitors. Nichicon capacitors can be used to provide an economical solution if space is available or a large bulk capacitance is already present on the input line. The number

of Sanyo (OS-CON) input capacitors required to handle various output currents are specified in Table 2.

Output Capacitor

To regulate the microprocessor's input voltage within 145 mV during 10-A load transients, a large output capacitance with low ESR is required. The output capacitor of the power supply and decoupling capacitors at the microprocessor must hold up the processor voltage until the power supply responds to the change. Even with fastest known switching solution, it still takes three 330-µF OS-CON capacitors to handle the load transient. If it weren't for the 10-A load transient, the output capacitor would not need a low ESR value. The fundamental output ripple current in a continuous step-down converter is much lower than the input ripple current. Maintaining voltage regulation during transients requires an ESR in the range of For microprocessors with lower transient 30 m Ω . requirements, the number of output and decoupling capacitors can be reduced. The lower transient requirements also allows greater consideration for Tantalum or Nichicon PL series capacitors.

Conclusion

The Si9140 synchronous Buck controller's ability to switch up to 1 MHz combined with a 25-MHz error amplifier provides the best solution in powering high- performance microprocessors. The high switching frequency reduces inductor size without compromising output ripple voltage. The wide converter bandwidth generated with the help of a 25-MHz error amplifier reduces the amount of decoupling capacitors required to handle the extreme transient requirement. The Si9140's synchronous fixed-frequency operation eliminates the pulse skipping mode that generates random unpredictable EMI/EMC problems in desktop and notebook computers. The synchronous rectification also allows the converter to operate in continuous current mode, independent of output load current. This preserves the wide closed-loop converter bandwidth required to meet the transient demand of the microprocessor as it transitions from stop clock and auto halt to active mode. The synchronous rectification improves the efficiency of the converter by substituting the much smaller I²R MOSFET loss for the VI diode loss. The need for heatsinking is eliminated by using low r_{DS(on)} TrenchFETs (Si4410DY and Si4435DY).

Legal Disclaimer Notice



Vishay

Notice

Specifications of the products displayed herein are subject to change without notice. Vishay Intertechnology, Inc., or anyone on its behalf, assumes no responsibility or liability for any errors or inaccuracies.

Information contained herein is intended to provide a product description only. No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted by this document. Except as provided in Vishay's terms and conditions of sale for such products, Vishay assumes no liability whatsoever, and disclaims any express or implied warranty, relating to sale and/or use of Vishay products including liability or warranties relating to fitness for a particular purpose, merchantability, or infringement of any patent, copyright, or other intellectual property right.


The products shown herein are not designed for use in medical, life-saving, or life-sustaining applications. Customers using or selling these products for use in such applications do so at their own risk and agree to fully indemnify Vishay for any damages resulting from such improper use or sale.

Document Number: 91000
Revision: 08-Apr-05
www.vishay.com



SOIC (NARROW): 16-LEAD (POWER IC ONLY)


JEDEC Part Number: MS-012

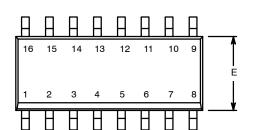


	MILLIMETERS		INC	HES	
Dim	Min	Max	Min	Max	
Α	1.35	1.75	0.053	0.069	
A ₁	0.10	0.20	0.004	0.008	
В	0.38	0.51	0.015	0.020	
С	0.18	0.23	0.007	0.009	
D	9.80	10.00	0.385	0.393	
E	3.80	4.00	0.149	0.157	
е	1.27	BSC	0.050	BSC	
Н	5.80	6.20	0.228	0.244	
L	0.50	0.93	0.020	0.037	
0	0°	8°	0°	8°	
ECN: \$ 40090 Poy A 02 Feb 04					

ECN: S-40080-Rev. A, 02-Feb-04

DWG: 5912

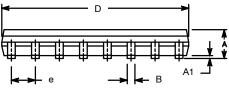


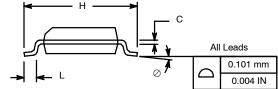



www.vishay.com 28-Jan-04



TSSOP: 16-LEAD

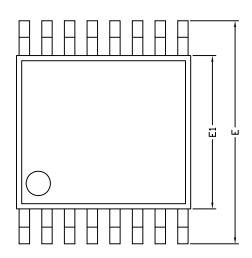

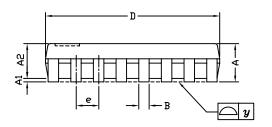

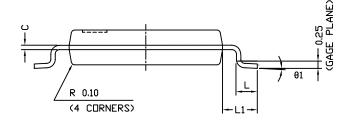


	DIMENSIONS IN MILLIMETERS			
Symbols	Min	Nom	Max	
А	-	1.10	1.20	
A1	0.05	0.10	0.15	
A2	-	1.00	1.05	
В	0.22	0.28	0.38	
С	-	0.127	-	
D	4.90	5.00	5.10	
E	6.10	6.40	6.70	
E1	4.30	4.40	4.50	
е	-	0.65	-	
L	0.50	0.60	0.70	
L1	0.90	1.00	1.10	
у	-	-	0.10	
θ1	0°	3°	6°	
FCN: S-61920-Rev. D. 23-	Oct-06			

DWG: 5624

Document Number: 74417 www.vishay.com 23-Oct-06



RECOMMENDED MINIMUM PAD FOR TSSOP-16

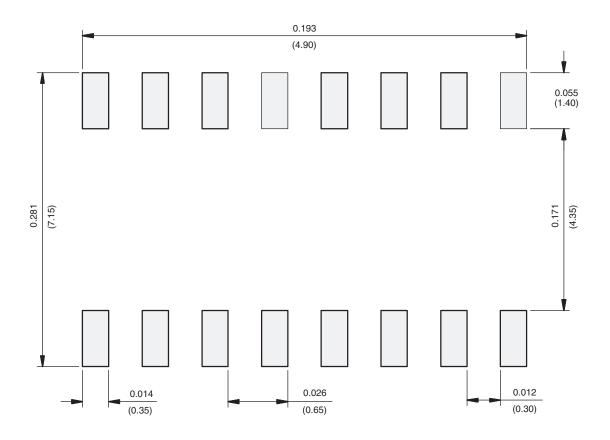

Recommended Minimum Pads Dimensions in inches (mm)



Legal Disclaimer Notice

Vishay

Disclaimer

ALL PRODUCT, PRODUCT SPECIFICATIONS AND DATA ARE SUBJECT TO CHANGE WITHOUT NOTICE TO IMPROVE RELIABILITY, FUNCTION OR DESIGN OR OTHERWISE.

Vishay Intertechnology, Inc., its affiliates, agents, and employees, and all persons acting on its or their behalf (collectively, "Vishay"), disclaim any and all liability for any errors, inaccuracies or incompleteness contained in any datasheet or in any other disclosure relating to any product.

Vishay makes no warranty, representation or guarantee regarding the suitability of the products for any particular purpose or the continuing production of any product. To the maximum extent permitted by applicable law, Vishay disclaims (i) any and all liability arising out of the application or use of any product, (ii) any and all liability, including without limitation special, consequential or incidental damages, and (iii) any and all implied warranties, including warranties of fitness for particular purpose, non-infringement and merchantability.

Statements regarding the suitability of products for certain types of applications are based on Vishay's knowledge of typical requirements that are often placed on Vishay products in generic applications. Such statements are not binding statements about the suitability of products for a particular application. It is the customer's responsibility to validate that a particular product with the properties described in the product specification is suitable for use in a particular application. Parameters provided in datasheets and/or specifications may vary in different applications and performance may vary over time. All operating parameters, including typical parameters, must be validated for each customer application by the customer's technical experts. Product specifications do not expand or otherwise modify Vishay's terms and conditions of purchase, including but not limited to the warranty expressed therein.

Except as expressly indicated in writing, Vishay products are not designed for use in medical, life-saving, or life-sustaining applications or for any other application in which the failure of the Vishay product could result in personal injury or death. Customers using or selling Vishay products not expressly indicated for use in such applications do so at their own risk and agree to fully indemnify and hold Vishay and its distributors harmless from and against any and all claims, liabilities, expenses and damages arising or resulting in connection with such use or sale, including attorneys fees, even if such claim alleges that Vishay or its distributor was negligent regarding the design or manufacture of the part. Please contact authorized Vishay personnel to obtain written terms and conditions regarding products designed for such applications.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted by this document or by any conduct of Vishay. Product names and markings noted herein may be trademarks of their respective owners.

Material Category Policy

Vishay Intertechnology, Inc. hereby certifies that all its products that are identified as RoHS-Compliant fulfill the definitions and restrictions defined under Directive 2011/65/EU of The European Parliament and of the Council of June 8, 2011 on the restriction of the use of certain hazardous substances in electrical and electronic equipment (EEE) - recast, unless otherwise specified as non-compliant.

Please note that some Vishay documentation may still make reference to RoHS Directive 2002/95/EC. We confirm that all the products identified as being compliant to Directive 2002/95/EC conform to Directive 2011/65/EU.